




## Lab3

Half Adder & Full Adder

# Half Adder

---

 



# Half Adder Design in SystemVerilog

- A **Half Adder** is the simplest type of digital adder that takes two input values and produces a **sum output** and a **carry output**. Unlike a **Full Adder**, a Half Adder does not have a **carry-in** input.

**Truth Table for Half Adder**

a	b	Sum (sum)	Carry (carry)
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

# SystemVerilog Code for Half Adder



C: > Users > Maryam > Desktop > Lab > fulladder > halfadder.sv > ...

```
1  module halfadder(  
2      input logic a, b,    // 1-bit inputs  
3      output logic sum,    // 1-bit sum output  
4      output logic carry   // 1-bit carry output  
5  );  
6  
7      // Sum is XOR of inputs  
8      assign sum = a ^ b;  
9  
10     // Carry is AND of inputs  
11     assign carry = a & b;  
12  
13  endmodule  
14
```

## Inputs:

`a, b` → These are **single-bit binary numbers** that will be added together.

## Outputs:

`sum` → Stores the **sum** of the two input bits.

`carry` → Stores the **carry-out** generated when both inputs are `1`.

### ✓ Sum Calculation ( `sum` )

- The `sum` is calculated using the **XOR ( `^` ) operator**:

$$sum = a \oplus b$$

### ✓ Carry Calculation ( `carry` )

- The `carry` is calculated using the **AND ( `&` ) operator**:

$$carry = a \cdot b$$

C: > Users > Maryam > Desktop > Lab > fulladder > halfadder.v > ...

```
1  `timescale 1ns / 1ps
2  module tb();
3
4      // Input and Output Variables
5      logic a, b;          // Inputs
6      logic sum, carry;    // Outputs
7
8      // Instantiate the Half Adder module
9      halfadder dut (
10         .a(a),
11         .b(b),
12         .sum(sum),
13         .carry(carry)
14     );
15
16     // Monitor signal values during execution
17     initial begin
18         $monitor("Time: %0t | a = %b, b = %b | sum = %b, carry = %b",
19             $time, a, b, sum, carry);
20     end
21
22     // Apply all possible input combinations
23     initial begin
24         a = 0; b = 0; #10;
25         a = 0; b = 1; #10;
26         a = 1; b = 0; #10;
27         a = 1; b = 1; #10;
28
29         // End of simulation
30         $finish;
31     end
32
33 endmodule
34
```

# Testbench Code



## Explanation of the Testbench

### ✓ Variable Definitions:

- `a, b` are single-bit inputs.
- `sum, carry` are the outputs computed by the Half Adder.

### ✓ Instantiation of the Half Adder Module:

- `halfadder dut (...)` creates an instance of the **main module** and connects its inputs and outputs.

### ✓ Displaying Values During Execution:

- `$monitor(...)` prints the values of `a, b, sum, carry` whenever a change occurs.

### ✓ Applying Test Cases for All Possible Conditions:


- The four possible input combinations `(a, b)` are tested:
  - `(0,0)`, `(0,1)`, `(1,0)`, `(1,1)`
- A **#10 delay** is added between each change in values.

### ✓ Ending the Simulation:

- After testing all cases, `$finish;` is executed to stop the simulation.


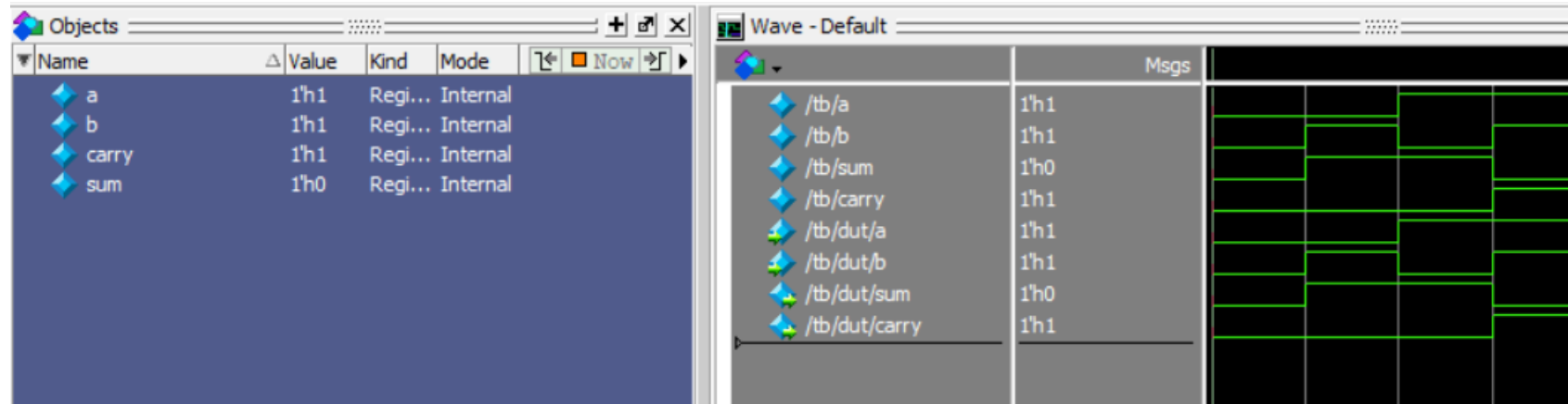
# Simulation Waveform of Half Adder in ModelSim



## Expected Output (Simulation Log)

```
bash
```

```
Time: 0 | a = 0, b = 0 | sum = 0, carry = 0
Time: 10 | a = 0, b = 1 | sum = 1, carry = 0
Time: 20 | a = 1, b = 0 | sum = 1, carry = 0
Time: 30 | a = 1, b = 1 | sum = 0, carry = 1
```

# Full Adder

---





# Full Adder Truth Table

Full Adder Truth Table


	a	b	c	Sum (s)	Carry (cout)
1	0	0	0	0	0
2	0	0	1	1	0
3	0	1	0	1	0
4	0	1	1	0	1
5	1	0	0	1	0
6	1	0	1	0	1
7	1	1	0	0	1
8	1	1	1	1	1





# SystemVerilog Code for Full Adder

```
fulladder sv Extension: SystemVerilog-1800-2012
C: > Users > Maryam > Desktop > Lab > fulladder > fulladder sv
1 module fulladder(
2     input logic a, b, c,
3     output logic s, cout
4 );
5
6 // Sum calculation using XOR
7 assign s = a ^ b ^ c;
8
9 // Carry-out calculation using AND & OR gates
10 assign cout = (a & b) | (a & c) | (b & c);
11
12 endmodule
13
```

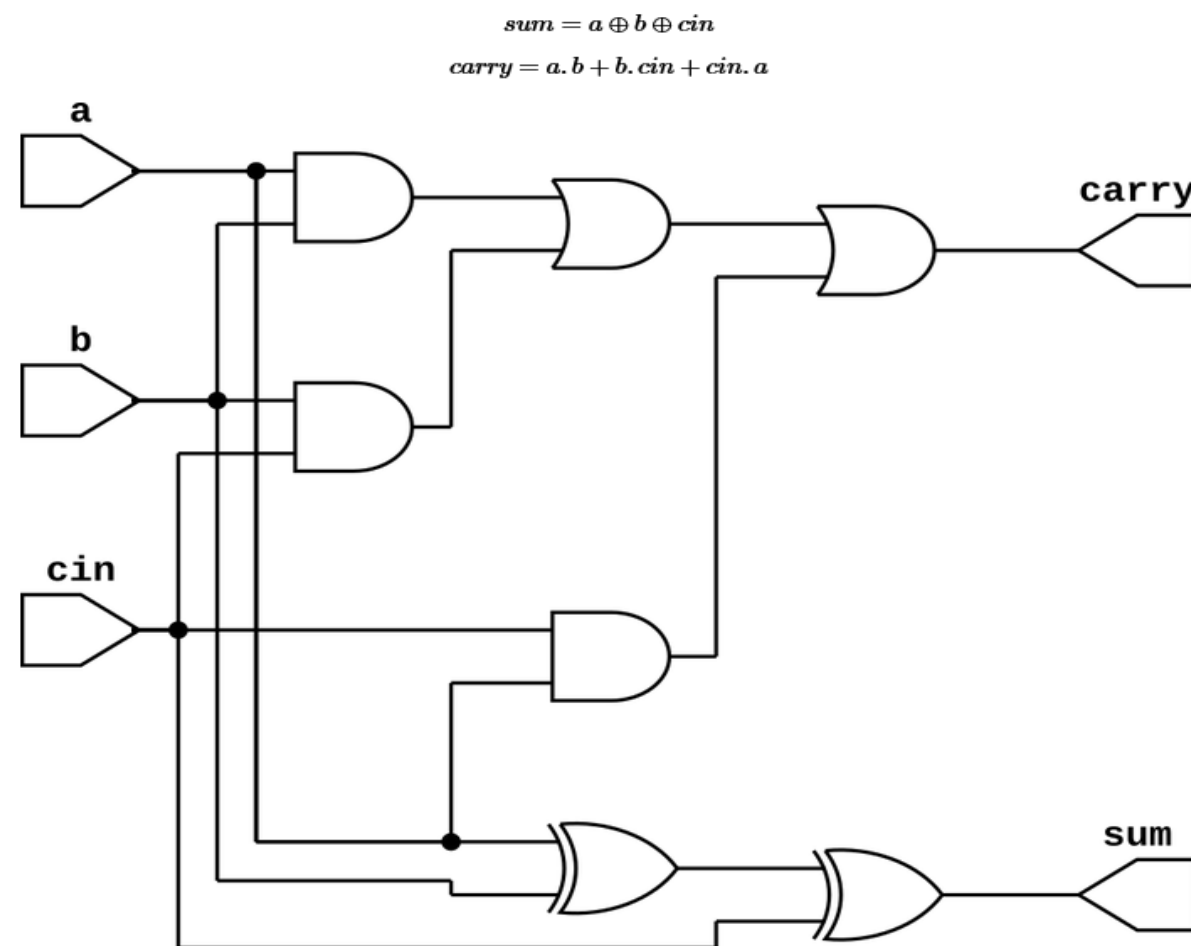

C: &gt; Users &gt; Maryam &gt; Desktop &gt; Lab &gt; fulladder &gt; fulladder\_tb.sv


```
1 | timescale 1ns / 1ps
2
3 module tb();
4
5     // Input and Output Variables
6     logic a, b, c;    // Inputs
7     logic s, cout;    // Outputs
8
9     // Instantiating the Full Adder module
10    fulladder dut (
11        .a(a),
12        .b(b),
13        .c(c),
14        .s(s),
15        .cout(cout)
16    );
17
18    // Displaying signal values during execution
19    initial begin
20        $monitor("Time: %0t | a = %b, b = %b, c = %b | s = %b, cout = %b",
21            | | | $time, a, b, c, s, cout);
22    end
23
24    // Applying all possible input combinations
25    initial begin
26        a = 0; b = 0; c = 0; #10;
27        a = 0; b = 0; c = 1; #10;
28        a = 0; b = 1; c = 0; #10;
29        a = 0; b = 1; c = 1; #10;
30        a = 1; b = 0; c = 0; #10;
31        a = 1; b = 0; c = 1; #10;
32        a = 1; b = 1; c = 0; #10;
33        a = 1; b = 1; c = 1; #10;
34
35        // End of simulation
36        $finish;
37    end
38
39    endmodule
40
```

# Testbench Code






# Full Adder Testbench Waveform Analysis

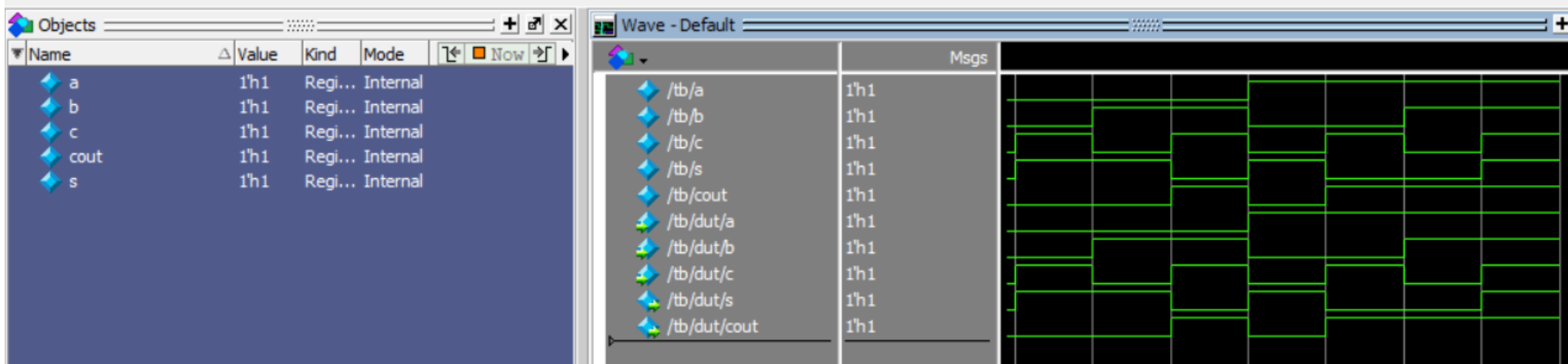


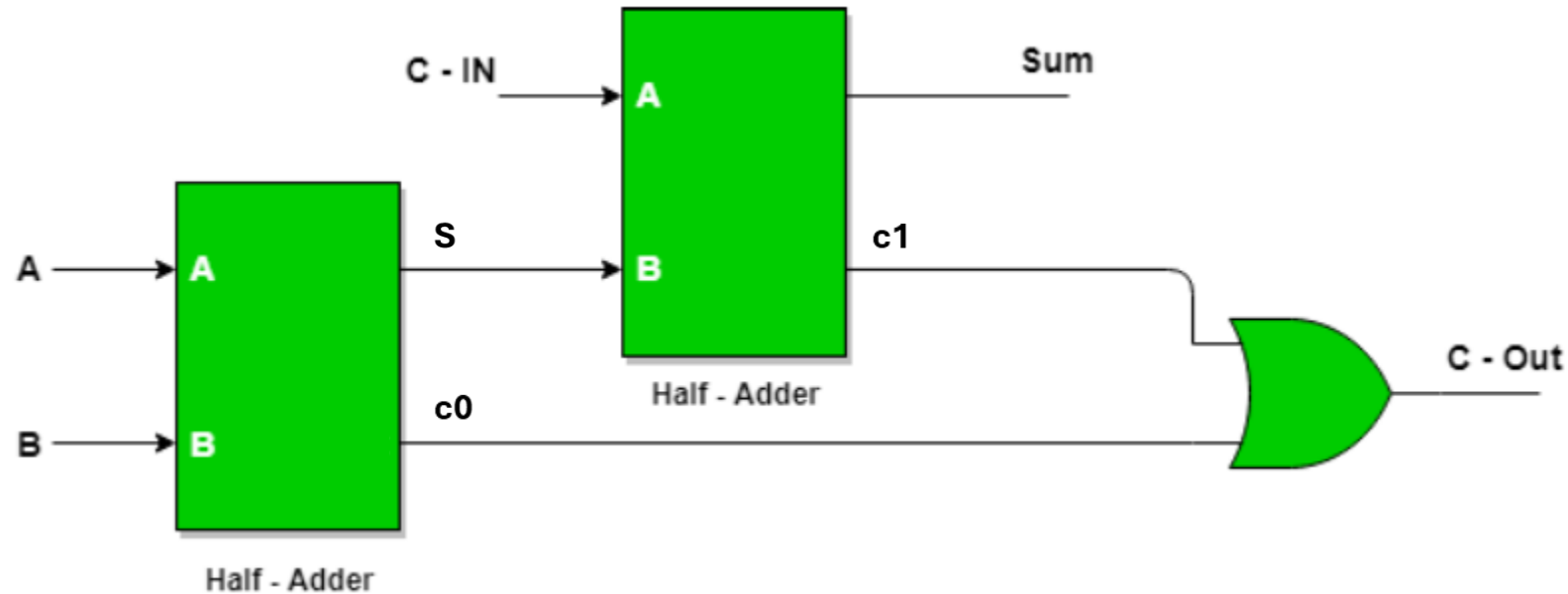
# Implementation of Full Adder using Half Adders

A Full Adder can be implemented using two Half Adders and an OR gate. With this logic circuit, two bits can be added together, taking a carry from the next lower order of magnitude, and sending a carry to the next higher order of magnitude



# Assignment: Implementing a Full Adder Using Two Half Adders

For the next assignment, please design a Full Adder using two Half Adders, as shown in the provided diagram.

- ☐ Your implementation should include:
- ☐ SystemVerilog Code for the Full Adder using two Half Adders.
- ☐ Testbench to verify the functionality.
- ☐ Truth Table covering all possible input combinations and expected outputs.
- ☐ Waveform Simulation to confirm correct operation.

Please ensure that your design follows the given structure and provides accurate results.